

# Homework # 1

**P1.4\*** The reference direction for  $i_{ab}$  points from  $a$  to  $b$ . Because  $i_{ab}$  has a negative value, the current is equivalent to positive charge moving opposite to the reference direction. Finally since electrons have negative charge, they are moving in the reference direction (i.e., from  $a$  to  $b$ ).

For a constant (dc) current, charge equals current times the time interval. Thus,  $Q = (5 \text{ A}) \times (3 \text{ s}) = 15 \text{ C}$ .

**P1.5\*** 
$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(2 + 3t) = 3 \text{ A}$$

**P1.7\*** 
$$Q = \int_0^{\infty} i(t) dt = \int_0^{\infty} 2e^{-t} dt = -2e^{-t} \Big|_0^{\infty} = 2 \text{ coulombs}$$

**P1.10\***  $Q = \text{current} \times \text{time} = (5 \text{ amperes}) \times (36,000 \text{ seconds}) = 1.8 \times 10^5 \text{ coulombs}$   
 $\text{Energy} = QV = (1.8 \times 10^5) \times (12) = 2.16 \times 10^6 \text{ joules}$

**P1.11\*** (a)  $P = -v_a i_a = -20 \text{ W}$  Energy is being supplied by the element.  
(b)  $P = v_b i_b = 50 \text{ W}$  Energy is being absorbed by the element.  
(c)  $P = -v_c i_c = 40 \text{ W}$  Energy is being absorbed by the element.

**P1.16\*** 
$$\text{Energy} = \frac{\text{Cost}}{\text{Rate}} = \frac{\$40}{0.1 \text{ \$/kWh}} = 400 \text{ kWh}$$

$$P = \frac{\text{Energy}}{\text{Time}} = \frac{400 \text{ kWh}}{30 \times 24 \text{ h}} = 555.5 \text{ W} \quad I = \frac{P}{V} = \frac{555.5}{120} = 4.630 \text{ A}$$

$$\text{Reduction} = \frac{40}{555.5} \times 100\% = 7.20\%$$

**P1.18\*** (a)  $P = 60 \text{ W}$  taken from element  $A$ .  
(b)  $P = 60 \text{ W}$  delivered to element  $A$ .  
(c)  $P = 60 \text{ W}$  taken from element  $A$ .

**P1.20\*** Elements  $A$  and  $B$  are in series. Also elements  $E$  and  $F$  are in series.

**P1.22\*** At the node joining elements  $A$  and  $B$ , we have  $i_a + i_b = 0$ . Thus,  $i_a = -2$  A. For the node at the top end of element  $C$ , we have  $i_b + i_c = 3$ . Thus,  $i_c = 1$  A. Finally, at the top right-hand corner node, we have  $3 + i_e = i_d$ . Thus,  $i_d = 4$  A. Elements  $A$  and  $B$  are in series.

**P1.23\*** We are given  $i_a = 2$  A,  $i_b = 3$  A,  $i_d = -5$  A, and  $i_h = 4$  A. Applying KCL, we find

$$\begin{aligned} i_c &= i_b - i_a = 1 \text{ A} & i_e &= i_c + i_h = 5 \text{ A} \\ i_f &= i_a + i_d = -3 \text{ A} & i_g &= i_f - i_h = -7 \text{ A} \end{aligned}$$

**P1.26\*** Summing voltages for the lower left-hand loop, we have  $-5 + v_a + 10 = 0$ , which yields  $v_a = -5$  V. Then for the top-most loop, we have  $v_c - 15 - v_a = 0$ , which yields  $v_c = 10$  V. Finally, writing KVL around the outside loop, we have  $-5 + v_c + v_b = 0$ , which yields  $v_b = -5$  V.

**P1.28\*** Applying KCL and KVL, we have


$$\begin{aligned} i_c &= i_a - i_d = 1 \text{ A} & i_b &= -i_a = -2 \text{ A} \\ v_b &= v_d - v_a = -6 \text{ V} & v_c &= v_d = 4 \text{ V} \end{aligned}$$

The power for each element is

$$\begin{aligned} P_A &= -v_a i_a = -20 \text{ W} & P_B &= v_b i_b = 12 \text{ W} \\ P_C &= v_c i_c = 4 \text{ W} & P_D &= v_d i_d = 4 \text{ W} \end{aligned}$$

Thus,  $P_A + P_B + P_C + P_D = 0$


**P1.30\***

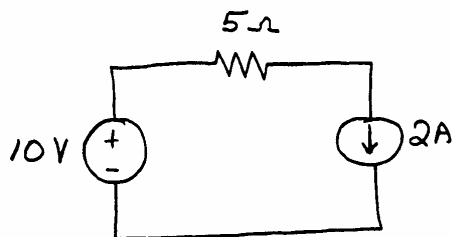

P1.36\*  $R = \frac{(V_1)^2}{P_1} = \frac{100^2}{100} = 100 \Omega$

$P_2 = \frac{(V_2)^2}{R} = \frac{90^2}{100} = 81 \text{ W}$  for a 19% reduction in power

P1.39\*

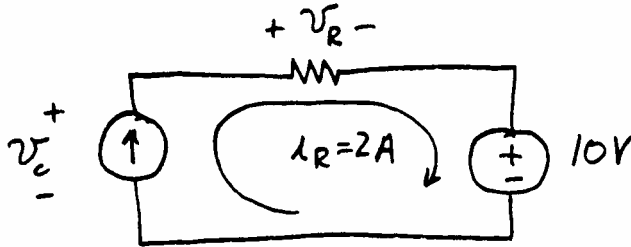

As shown above, the 2 A current circulates clockwise through all three elements in the circuit. Applying KVL, we have


$$v_c = v_R + 10 = 5i_R + 10 = 20 \text{ V}$$

$P_{\text{current-source}} = -v_c i_R = -40 \text{ W}$ . Thus, the current source delivers power.

$P_R = (i_R)^2 R = 2^2 \times 5 = 20 \text{ W}$ . The resistor absorbs power.

$P_{\text{voltage-source}} = 10 \times i_R = 20 \text{ W}$ . The voltage source absorbs power.

P1.41\*

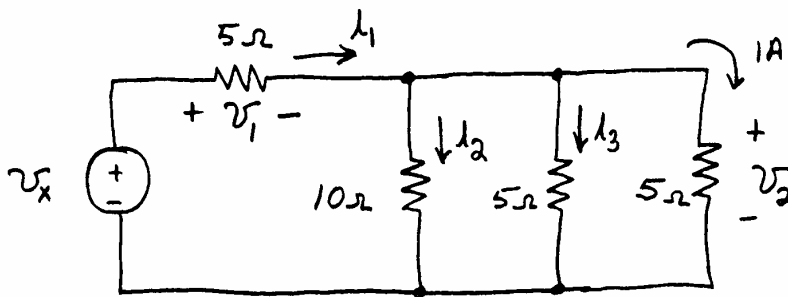

Applying Ohm's law, we have  $v_2 = (5\Omega) \times (1 \text{ A}) = 5 \text{ V}$ . However,  $v_2$  is the voltage across all three resistors that are in parallel. Thus,

$i_3 = \frac{v_2}{5} = 1 \text{ A}$ , and  $i_2 = \frac{v_2}{10} = 0.5 \text{ A}$ . Applying KCL, we have


$i_1 = i_2 + i_3 + 1 = 2.5 \text{ A}$ . By Ohm's law:  $v_1 = 5i_1 = 12.5 \text{ V}$ . Finally using KVL, we have  $v_x = v_1 + v_2 = 17.5 \text{ V}$ .

- P1.42\*** (a) Applying KVL, we have  $10 = v_x + 5v_x$ , which yields  $v_x = 10/6 = 1.667 \text{ V}$   
 (b)  $i_x = v_x / 3 = 0.5556 \text{ A}$   
 (c)  $P_{\text{voltage-source}} = -10i_x = -5.556 \text{ W}$ . (This represents power delivered by the voltage source.)

$$P_R = 3(i_x)^2 = 0.926 \text{ W (absorbed)}$$

$$P_{\text{controlled-source}} = 5v_x i_x = 4.63 \text{ W (absorbed)}$$

**P1.44\***

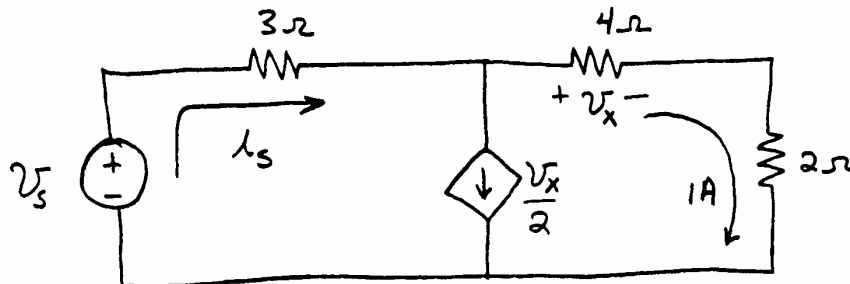

$$v_x = (4 \Omega) \times (1 \text{ A}) = 4 \text{ V}$$

$$i_s = v_x / 2 + 1 = 3 \text{ A}$$

Applying KVL around the outside of the circuit:

$$v_s = 3i_s + 4 + 2 = 15 \text{ V}$$