

Homework # 1

P1.6* The reference direction for i_{ab} points from a to b . Because i_{ab} has a negative value, the current is equivalent to positive charge moving opposite to the reference direction. Finally since electrons have negative charge, they are moving in the reference direction (i.e., from a to b).

For a constant (dc) current, charge equals current times the time interval. Thus, $Q = (5 \text{ A}) \times (3 \text{ s}) = 15 \text{ C}$.

P1.7*
$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(2 + 3t) = 3 \text{ A}$$

P1.9*
$$Q = \int_0^{\infty} i(t) dt = \int_0^{\infty} 2e^{-t} dt = -2e^{-t} \Big|_0^{\infty} = 2 \text{ coulombs}$$

P1.13* $Q = \text{current} \times \text{time} = (5 \text{ amperes}) \times (36,000 \text{ seconds}) = 1.8 \times 10^5 \text{ coulombs}$
 $\text{Energy} = QV = (1.8 \times 10^5) \times (12) = 2.16 \times 10^6 \text{ joules}$

P1.14* (a) $P = -v_a i_a = -20 \text{ W}$ Energy is being supplied by the element.
(b) $P = v_b i_b = 50 \text{ W}$ Energy is being absorbed by the element.
(c) $P = -v_c i_c = 40 \text{ W}$ Energy is being absorbed by the element.

P1.19*
$$\text{Energy} = \frac{\text{Cost}}{\text{Rate}} = \frac{\$40}{0.1 \text{ \$/kWh}} = 400 \text{ kWh}$$

$$P = \frac{\text{Energy}}{\text{Time}} = \frac{400 \text{ kWh}}{30 \times 24 \text{ h}} = 555.5 \text{ W} \quad I = \frac{P}{V} = \frac{555.5}{120} = 4.630 \text{ A}$$

$$\text{Reduction} = \frac{40}{555.5} \times 100\% = 7.20\%$$

P1.21* (a) $P = 60 \text{ W}$ taken from element A .
(b) $P = 60 \text{ W}$ delivered to element A .
(c) $P = 60 \text{ W}$ taken from element A .

P1.26* Elements A and B are in series. Also elements E and F are in series.

P1.28* At the node joining elements A and B , we have $i_a + i_b = 0$. Thus, $i_a = -2$ A. For the node at the top end of element C , we have $i_b + i_c = 3$. Thus, $i_c = 1$ A. Finally, at the top right-hand corner node, we have $3 + i_e = i_d$. Thus, $i_d = 4$ A. Elements A and B are in series.

P1.29* We are given $i_a = 2$ A, $i_b = 3$ A, $i_d = -5$ A, and $i_h = 4$ A. Applying KCL, we find

$$\begin{aligned} i_c &= i_b - i_a = 1 \text{ A} & i_e &= i_c + i_h = 5 \text{ A} \\ i_f &= i_a + i_d = -3 \text{ A} & i_g &= i_f - i_h = -7 \text{ A} \end{aligned}$$

P1.32* Summing voltages for the lower left-hand loop, we have $-5 + v_a + 10 = 0$, which yields $v_a = -5$ V. Then for the top-most loop, we have $v_c - 15 - v_a = 0$, which yields $v_c = 10$ V. Finally, writing KVL around the outside loop, we have $-5 + v_c + v_b = 0$, which yields $v_b = -5$ V.

P1.34* Applying KCL and KVL, we have


$$\begin{aligned} i_c &= i_a - i_d = 1 \text{ A} & i_b &= -i_a = -2 \text{ A} \\ v_b &= v_d - v_a = -6 \text{ V} & v_c &= v_d = 4 \text{ V} \end{aligned}$$

The power for each element is

$$\begin{aligned} P_A &= -v_a i_a = -20 \text{ W} & P_B &= v_b i_b = 12 \text{ W} \\ P_C &= v_c i_c = 4 \text{ W} & P_D &= v_d i_d = 4 \text{ W} \end{aligned}$$

Thus, $P_A + P_B + P_C + P_D = 0$


P1.37*

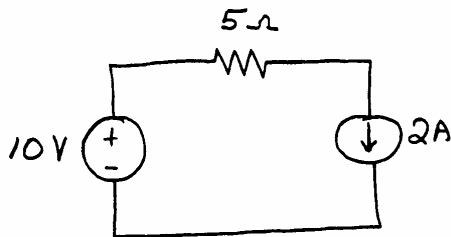

P1.43* $R = \frac{(V_1)^2}{P_1} = \frac{100^2}{100} = 100 \Omega$

$P_2 = \frac{(V_2)^2}{R} = \frac{90^2}{100} = 81 \text{ W}$ for a 19% reduction in power

P1.48*

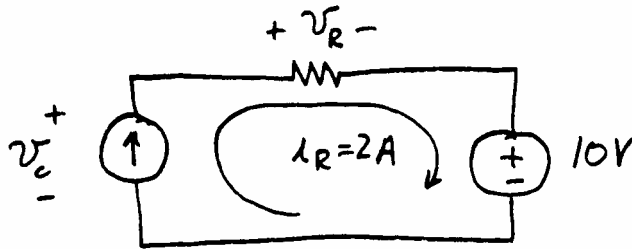

As shown above, the 2 A current circulates clockwise through all three elements in the circuit. Applying KVL, we have


$$v_c = v_R + 10 = 5i_R + 10 = 20 \text{ V}$$

$P_{\text{current-source}} = -v_c i_R = -40 \text{ W}$. Thus, the current source delivers power.

$P_R = (i_R)^2 R = 2^2 \times 5 = 20 \text{ W}$. The resistor absorbs power.

$P_{\text{voltage-source}} = 10 \times i_R = 20 \text{ W}$. The voltage source absorbs power.

P1.50*

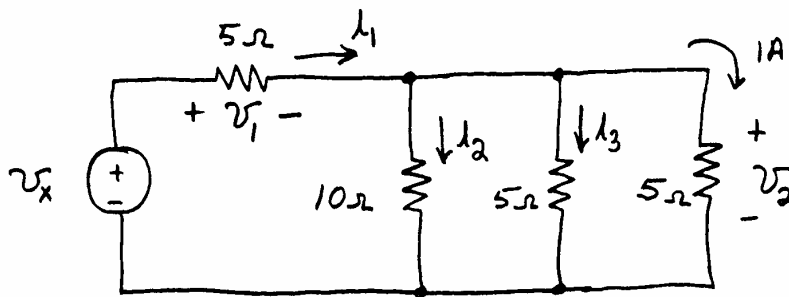

Applying Ohm's law, we have $v_2 = (5\Omega) \times (1A) = 5 \text{ V}$. However, v_2 is the voltage across all three resistors that are in parallel. Thus,

$i_3 = \frac{v_2}{5} = 1 \text{ A}$, and $i_2 = \frac{v_2}{10} = 0.5 \text{ A}$. Applying KCL, we have


$i_1 = i_2 + i_3 + 1 = 2.5 \text{ A}$. By Ohm's law: $v_1 = 5i_1 = 12.5 \text{ V}$. Finally using KVL, we have $v_x = v_1 + v_2 = 17.5 \text{ V}$.

- P1.52*** (a) Applying KVL, we have $10 = v_x + 5v_x$, which yields $v_x = 10/6 = 1.667 \text{ V}$
 (b) $i_x = v_x / 3 = 0.5556 \text{ A}$
 (c) $P_{\text{voltage-source}} = -10i_x = -5.556 \text{ W}$. (This represents power delivered by the voltage source.)

$$P_R = 3(i_x)^2 = 0.926 \text{ W (absorbed)}$$

$$P_{\text{controlled-source}} = 5v_x i_x = 4.63 \text{ W (absorbed)}$$

P1.57*

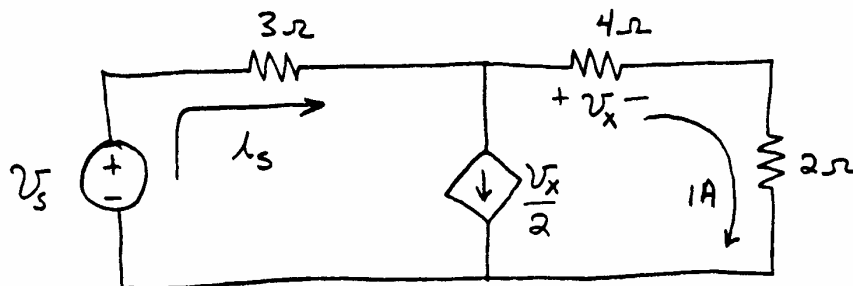

$$v_x = (4 \Omega) \times (1 \text{ A}) = 4 \text{ V}$$

$$i_s = v_x / 2 + 1 = 3 \text{ A}$$

Applying KVL around the outside of the circuit:

$$v_s = 3i_s + 4 + 2 = 15 \text{ V}$$