

Homework # 3

$$\text{P2.29*} \quad v_1 = \frac{R_1}{R_1 + R_2 + R_3} \times v_s = 5 \text{ V} \quad v_2 = \frac{R_2}{R_1 + R_2 + R_3} \times v_s = 7 \text{ V}$$
$$v_3 = \frac{R_3}{R_1 + R_2 + R_3} \times v_s = 13 \text{ V}$$

$$\text{P2.30*} \quad i_1 = \frac{R_2}{R_1 + R_2} i_s = 1 \text{ A} \quad i_2 = \frac{R_1}{R_1 + R_2} i_s = 2 \text{ A}$$

$$\text{P2.34*} \quad v = 0.1 \text{ mA} \times R_w = 50 \text{ mV}$$

$$R_g = \frac{50 \text{ mV}}{2 \text{ A} - 0.1 \text{ mA}} = 25 \text{ m}\Omega$$

P2.36* Combining R_2 and R_3 , we have an equivalent resistance

$$R_{eq} = \frac{1}{1/R_2 + 1/R_3} = 10 \Omega. \text{ Then using the voltage-division principle, we have}$$

$$v = \frac{R_{eq}}{R_1 + R_{eq}} \times v_s = \frac{10}{20 + 10} \times 10 = 3.333 \text{ V}.$$

$$\text{P2.38*} \quad \text{At node 1 we have: } \frac{v_1}{20} + \frac{v_1 - v_2}{10} = 1$$

$$\text{At node 2 we have: } \frac{v_2}{5} + \frac{v_2 - v_1}{10} = 2$$

In standard form the equations become

$$0.15v_1 - 0.1v_2 = 1$$

$$-0.1v_1 + 0.3v_2 = 2$$

Solving, we find $v_1 = 14.29 \text{ V}$ and $v_2 = 11.43 \text{ V}$.

$$\text{Then we have } i_1 = \frac{v_1 - v_2}{10} = 0.2857 \text{ A}.$$

P2.39* Writing a KVL equation, we have $v_1 - v_2 = 10$.

$$\text{At the reference node, we write a KCL equation: } \frac{v_1}{5} + \frac{v_2}{10} = 1.$$

Solving, we find $v_1 = 6.667$ and $v_2 = -3.333$.

Then, writing KCL at node 1, we have $i_s = \frac{v_2 - v_1}{5} - \frac{v_1}{5} = -3.333 \text{ A}$.

P2.46* First, we can write: $i_x = \frac{v_1 - v_2}{5}$.

Then, writing KCL equations at nodes 1 and 2, we have:

$$\frac{v_1}{10} + i_x = 1 \quad \text{and} \quad \frac{v_2}{20} + 0.5i_x - i_x = 0$$

Substituting for i_x and simplifying, we have

$$\begin{aligned} 0.3v_1 - 0.2v_2 &= 1 \\ -0.1v_1 + 0.15v_2 &= 0 \end{aligned}$$

Solving, we have $v_1 = 6$ and $v_2 = 4$.

Then, we have $i_x = \frac{v_1 - v_2}{5} = 0.4 \text{ A}$.

P2.48* $v_x = v_2 - v_1$

Writing KCL at nodes 1 and 2:

$$\frac{v_1}{5} + \frac{v_1 - 2v_x}{15} + \frac{v_1 - v_2}{10} = 1$$

$$\frac{v_2}{5} + \frac{v_2 - 2v_x}{10} + \frac{v_2 - v_1}{10} = 2$$

Substituting and simplifying, we have

$$15v_1 - 7v_2 = 30 \quad \text{and} \quad v_1 + 2v_2 = 20.$$

Solving, we find $v_1 = 5.405$ and $v_2 = 7.297$.

P2.52* Writing KVL equations around each mesh we have


$$5i_1 + 15(i_1 - i_2) = 20 \quad \text{and} \quad 15(i_2 - i_1) + 10i_2 = 10$$

Putting the equations into standard form we have

$$20i_1 - 15i_2 = 20 \quad \text{and} \quad -15i_1 + 25i_2 = 10$$

Solving we obtain $i_1 = 2.364 \text{ A}$ and $i_2 = 1.818 \text{ A}$.

P2.54*

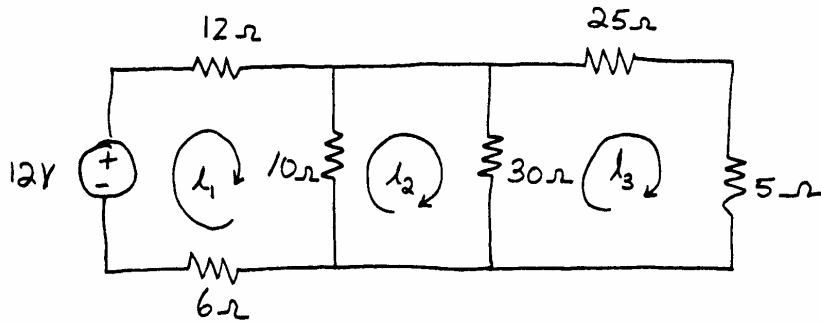

Writing and simplifying the mesh-current equations, we have:


$$\begin{aligned} 28i_1 - 10i_2 &= 12 \\ -10i_1 + 40i_2 - 30i_3 &= 0 \\ -30i_2 + 60i_3 &= 0 \end{aligned}$$

Solving, we obtain

$$i_1 = 0.500 \quad i_2 = 0.200 \quad i_3 = 0.100$$

Thus, $v_2 = 5i_3 = 0.500 \text{ V}$.

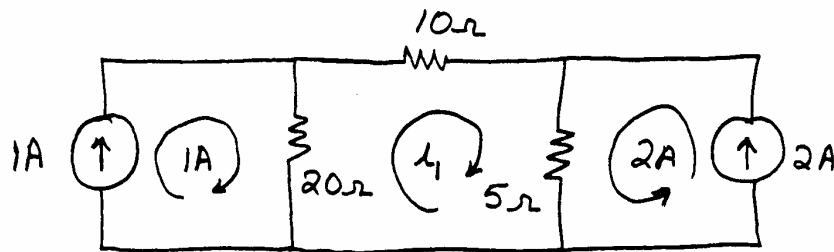P2.61* Because of the current sources, two of the mesh currents are known.



Writing a KVL equation around the middle loop we have


$$20(i_1 - 1) + 10i_1 + 5(i_1 + 2) = 0$$

Solving, we find $i_1 = 0.2857$.


P2.65* First, we write a node voltage equation to solve for the open-circuit voltage:

$$\frac{v_{oc} - 10}{10} + \frac{v_{oc}}{5} = 1$$


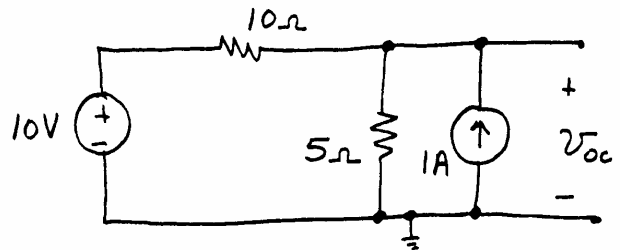
Solving, we find $v_{oc} = 6.667 \text{ V}$.



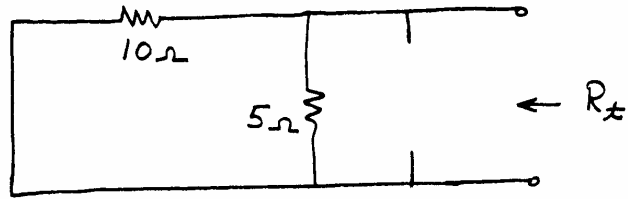
Then zeroing the sources, we have this circuit:



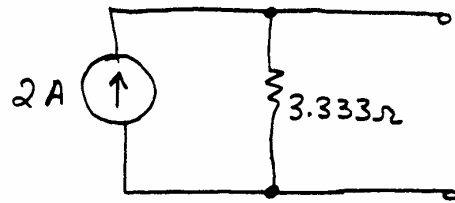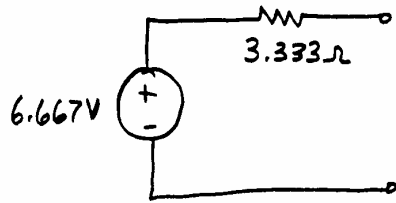Thus, $R_T = \frac{1}{1/10 + 1/5} = 3.333 \Omega$. The Thevenin and Norton equivalents are:



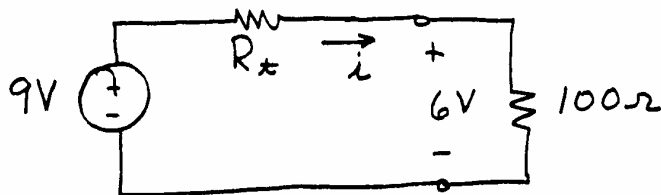P2.67* The equivalent circuit of the battery with the resistance connected is




$$i = 6/100 = 0.06 \text{ A}$$

$$R_T = \frac{9-6}{0.06} = 50 \Omega$$

P2.75* To maximize the power to R_L , we must maximize the voltage across it. Thus we need to have $R_T = 0$. The maximum power is


$$P_{\max} = \frac{20^2}{5} = 80 \text{ W}$$

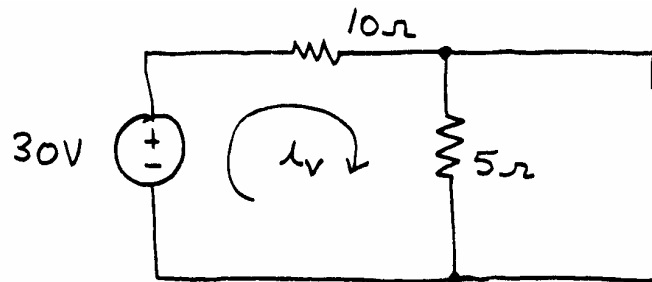P2.78* First, we zero the current source and find the current due to the voltage source.



$$i_v = 30/15 = 2 \text{ A}$$

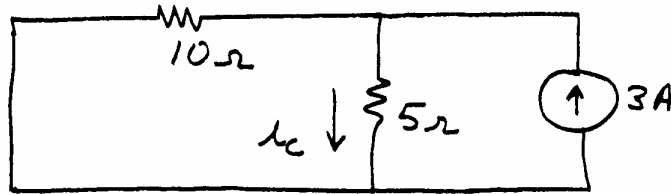Then we zero the voltage source and use the current-division principle to find the current due to the current source.




$$i_c = 3 \frac{10}{5 + 10} = 2 \text{ A}$$

Finally, the total current is the sum of the contributions from each source.


$$i = i_v + i_c = 4 \text{ A}$$

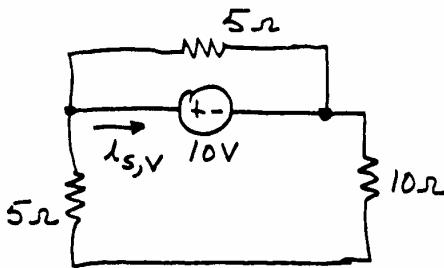P2.81* The circuits with only one source active at a time are:



$$R_{eq} = \frac{1}{1/5 + 1/15} = 3.75 \Omega$$
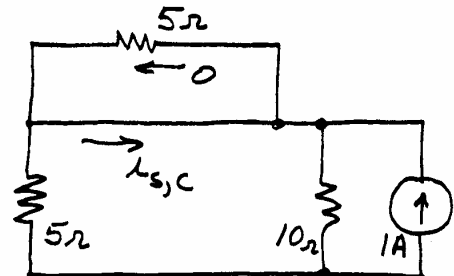
$$i_{s,v} = -\frac{10 \text{ V}}{R_{eq}} = -2.667 \text{ A}$$




$$i_{s,c} = -1 \frac{10}{10 + 5} = -0.667 \text{ A}$$

Then the total current due to both sources is $i_s = i_{s,v} + i_{s,c} = -3.333 \text{ A}$.

P2.87* (a) Rearranging Equation 2.80, we have

$$R_3 = \frac{R_1}{R_2} R_x = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega} \times 5932 = 5932 \Omega$$

(b) The circuit is:

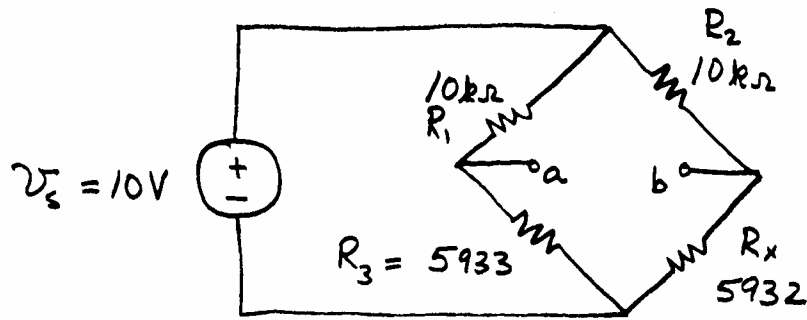


The Thevenin resistance is

$$R_t = \frac{1}{1/R_3 + 1/R_1} + \frac{1}{1/R_2 + 1/R_x} = 7447 \Omega$$

The Thevenin voltage is

$$V_t = V_s \frac{R_3}{R_1 + R_3} - V_s \frac{R_x}{R_x + R_2} = 0.3939 \text{ mV}$$

Thus, the equivalent circuit is:

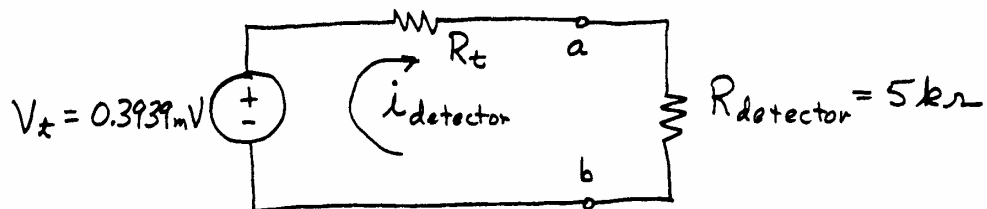

$$i_{\text{detector}} = \frac{V_t}{R_t + R_{\text{detector}}} = 31.65 \times 10^{-9} \text{ A}$$

Thus the detector must be sensitive to very small currents if the bridge is to be accurately balanced.