

EE100B  
Experiment 4

**Basic Output-Stage Circuits**


College of Engineering  
University of California, Riverside

**Objective**


To familiarize with basic output-stage topologies. Class-A and Class-B examples will be explored.

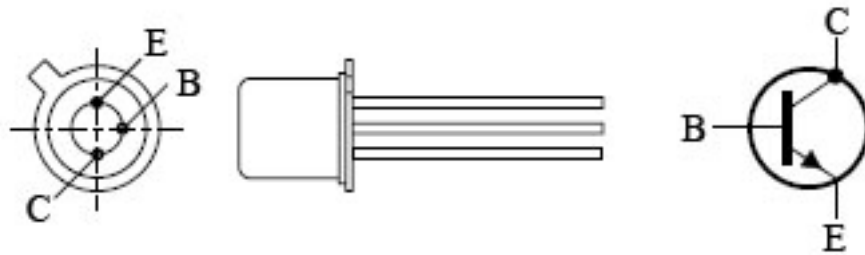**Equipment**

2 non BJTs (2N2222), 1 pnp BJT (2N3906), 1 diode (1N914), resistors (100Ω, 1kΩ, 10kΩ), function generator, oscilloscope, digital multimeter, DC power supply, breadboard



2N2222 npn transistor

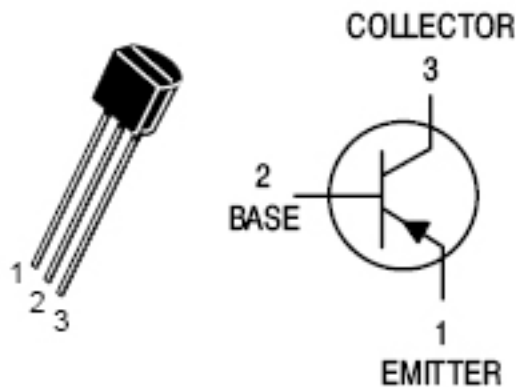

2N3906 pnp transistor

**Figure L4.1** BJT Base Diagrams

## Prelab

Read the sections of your textbook relevant to this laboratory session.


### The Class-A Follower

#### 1. DC Bias

For the circuit shown in Figure L4.2, assuming that  $D_1$  and  $Q_2$  are matched, what current flows into the emitter of  $Q_1$ , assuming that  $\beta$  is very high? If  $R_2$  is changed to a  $1\text{k}\Omega$  resistor, what will  $I_{E1}$  become? If  $\beta=100$ , what voltage drop occurs in  $R_1$ ?

#### 2. Signal Operation

For the circuit shown in Figure L4.2, what are the upper and lower limits of  $v_B$  for a load of  $R_L = 10\text{k}\Omega$ , assuming that  $\beta$  is very high?

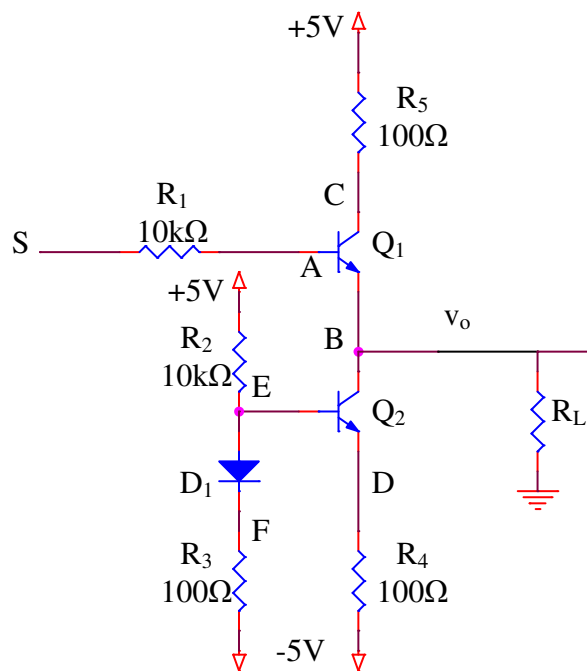

**Figure L4.2** A Class-A BJT Follower with Emitter-Current Bias


## The Class-B Follower

### 1. DC Bias

For the circuit as shown in Figure L4.3, what emitter current flows into each transistor for high  $\beta$ , with  $R_L = 10\text{k}\Omega$ , when  $v_S = +3\text{V}$ ,  $0\text{V}$ , and  $-7\text{V}$ ?

### 2. Signal Operation

For the circuit as shown in Figure L4.3, sketch the waveform at node B, with  $v_S$  being a triangle wave of  $\pm 1\text{V}$  amplitude, and  $R_L = 10\text{k}\Omega$ . Assume  $\beta$  is high and  $|V_{BE}| = 0.7\text{V}$ . What are the largest unclipped signal peaks at node B with  $R_L = 10\text{k}\Omega$ , if  $\beta = 100$ ? (Be careful to include  $R_2$ ,  $R_3$ ).

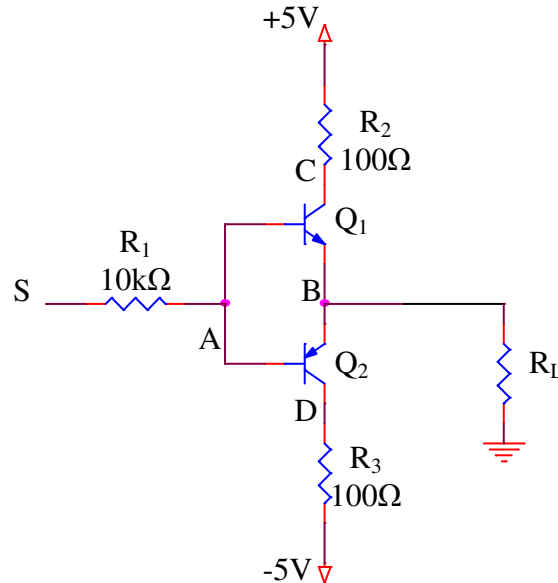

**Figure L4.3** A Class-B Complementary BJT Output Stage

## Laboratory Procedure

### The Class-A Follower

In the circuit shown in Figure L4.2,  $Q_2$  and the associated components supply a constant current to the follower  $Q_1$ . Resistors  $R_3$  and  $R_4$  serve to equalize the currents in  $D_1$  and  $Q_2$  whose junctions are likely to be quite different in size. Resistor  $R_5$  serves simply to allow one to monitor the bias current directly. Resistor  $R_1$  represents the internal resistance of a typical signal source.

### 1. DC Bias

Assemble the circuit as shown in Figure L4.2 with S grounded and no load connected to node B. Adjust the supplies to  $\pm 5\text{V}$  as closely as you can. Measure the voltages at nodes A, B, C, D, E and F. Estimate the collector current of  $Q_1$  and its  $\beta$ .

Consider  $\beta$  and  $r_e$  at the current levels you have measured. Notice that the currents in  $D_1$  and  $Q_2$  are nearly the same (due to  $R_3$  and  $R_4$ ).

### 2. Signal Operation

Change the circuit in Figure L4.2 to  $R_2 = 1\text{k}\Omega$ , a load  $R_L = 10\text{k}\Omega$ , and node S connected to a function generator providing a  $0.2\text{ V}_{pp}$  triangle wave at  $1\text{ kHz}$ . With the oscilloscope, measure the voltages at nodes S, A and B. Calculate the voltage gains from S to B ( $v_B/v_S$ ) and A to B ( $v_B/v_A$ ). Also measure the input resistance at A.

While observing nodes S and B, with both oscilloscope channels direct-coupled with zero volts at the screen center, raise the input voltage until first the output waveform is clipped at one peak, then the other. What are the peak output voltages at each case?

Consider the values of input resistance and gain you find here in view of the conclusions you could draw using the data obtained from the part 1 (DC Bias) above. As well, correlate the peak limiting values with voltage measurements taken in part 1 above.

### The Class-B Follower

#### 1. DC Bias

Assemble the circuit in Figure L4.3 with node S grounded,  $R_L=10k\Omega$ , and supplies at  $\pm 5V$ . Use the multimeter to measure the voltages at nodes A, B, C and D, to verify that there is no standing bias current in the circuit.

#### 2. Signal Operation

With a  $0.2 V_{pp}$  triangle wave applied to node S initially and a load  $10k\Omega$  connected to node B, measure nodes S, A and B with the two-channel oscilloscope. With nodes S and B displayed on an oscilloscope, slowly increase the input signal, noting the peak value of the signal at S for which output at node B is just noticeable. Continue to increase the input amplitude until a  $1V_{pp}$  output is observed at S and A. Observing node B, increase the input signal until the output peaks just begin to limit. Note their value and the corresponding peak values at nodes S and A. Estimate device  $\beta$  at the peaks. What have you discovered?