

Homework 1

1.5. (Section 1.2) Convert the following binary numbers to decimal numbers:

- a. 100
- b. 1011
- c. 000000000001
- d. 111111
- e. 101010

1.8. (Section 1.2) Convert the following decimal numbers to binary numbers using the subtraction method:

- a. 9
- b. 15
- c. 32
- d. 140

1.15. (Section 1.2) Convert the following binary numbers to hexadecimal:

- a. 11110000
- b. 11111111
- c. 01011010
- d. 1001101101101

1.18. (Section 1.2) Convert the following hexadecimal numbers to binary:

- a. FF
- b. F0A2
- c. 0F100
- d. 100

2.11. (Section 2.4) We want to design a system that sounds a buzzer inside our home whenever motion outside is detected at night. Assuming we have a motion sensor with output M that indicates whether motion is detected (M=1 means motion detected) and a light sensor with output L that indicates if light is detected (L means light is detected). The buzzer inside the home has a single input B that when 1 creates a loud warning sound. Using AND, OR, and NOT gates, create a simple digital circuit to implement the motion detector at night system.

2.13. (Section 2.4) Convert each of the following equations directly to gate-level circuits:

- a. $F = ab + b'$
- b. $F = abc + def + acf + f'$
- c. $F = ((a + b)*(c)) + (d + e + fg)$

2.18. (Section 2.5) Use algebraic manipulation to convert the following equation to sum-of-products form: $F = a(b + c)(d') + ac'(b + d)$

2.24. (Section 2.6) Convert the following Boolean equations to a truth table.

- a. $F(a,b,c) = a'b + ac$
- b. $F(a,b,c) = abc + a'bc + a'c'$
- c. $F(a,b,c) = abc + a'b'c' + b'c$
- d. $F(a,b,c,d) = a'bcd + ab'cd + abc'd + abcd'$

2.28. (Section 2.6) Convert the function F shown in the truth table in Table 2.6 to an equation. Don't minimize the equation.

Table 2.6: Truth table.

a	b	c	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

2.29. (Section 2.6) Use algebraic manipulation to minimize the equation obtained in Exercise 2.28.